

COMP 122/L Lecture 27

Kyle Dewey

Outline

- Finite state machines


Finite State Machines

Finite State Machines


Basic idea: computation is done via traversal of **states**, where the states are known ahead of time.

Finite State Machines

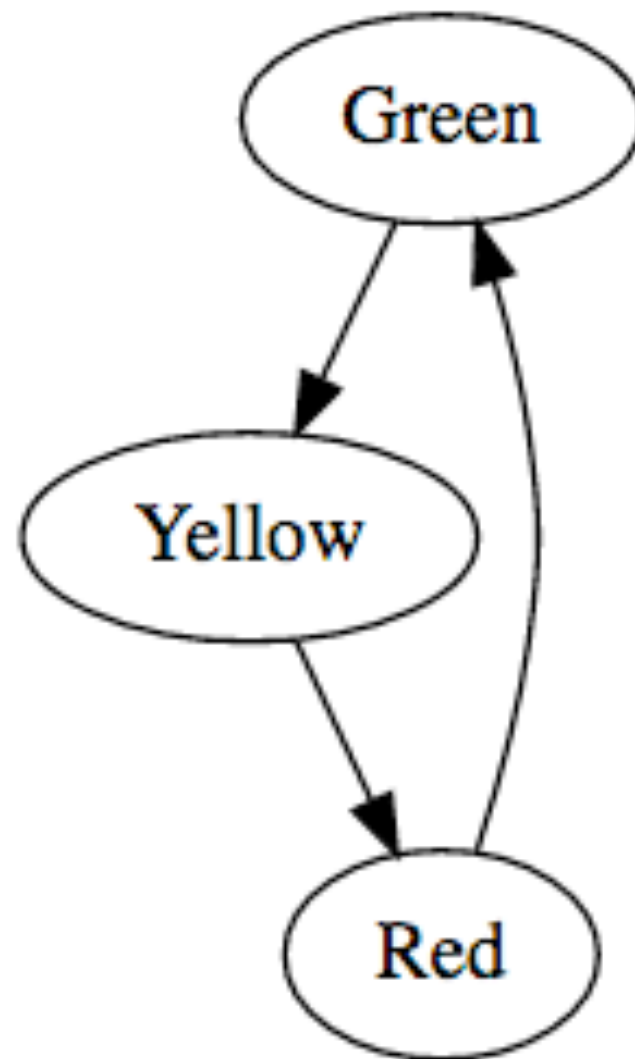
Basic idea: computation is done via traversal of **states**, where the states are known ahead of time.



Example: Lock and Key

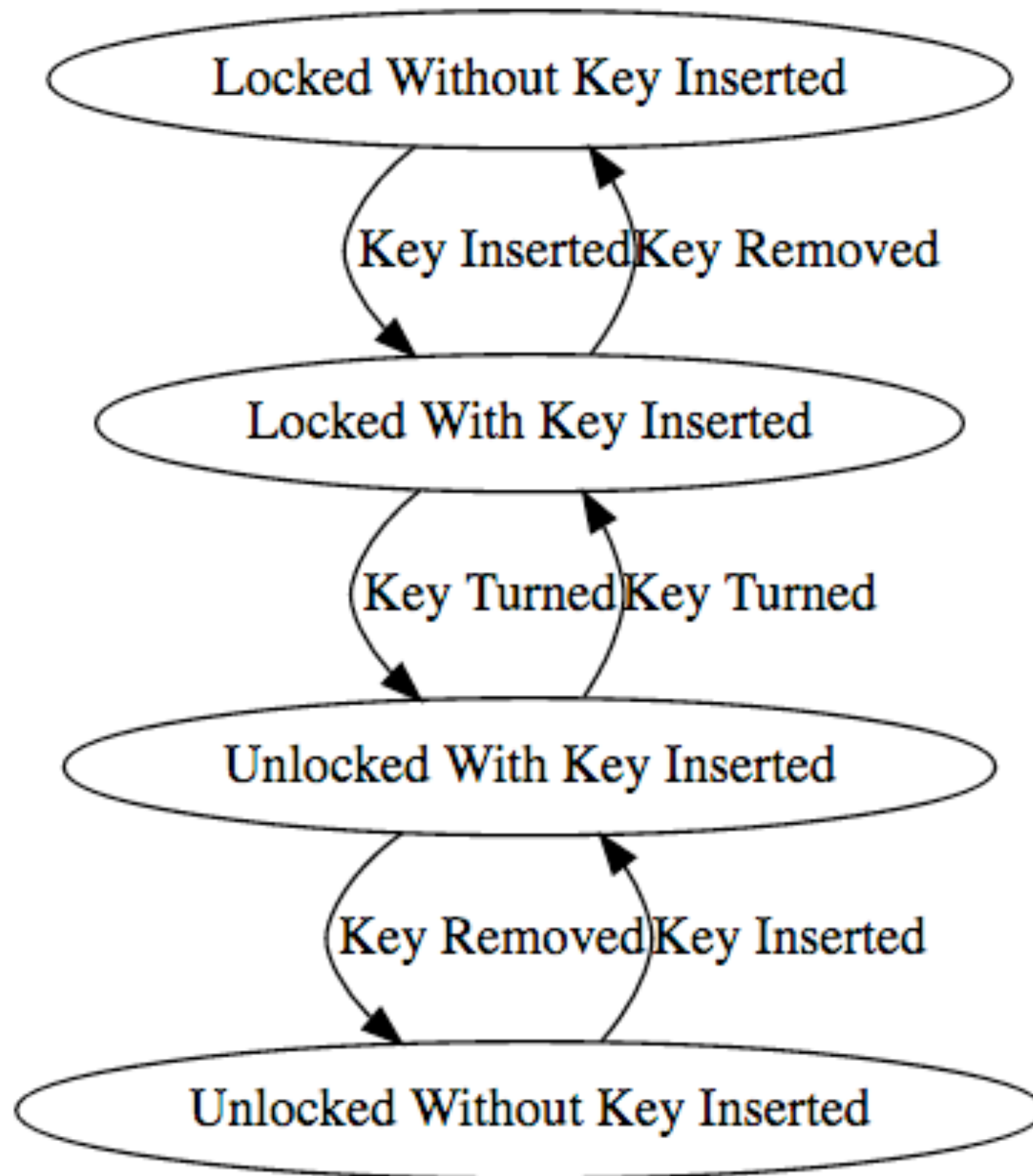

Example: Counting Change

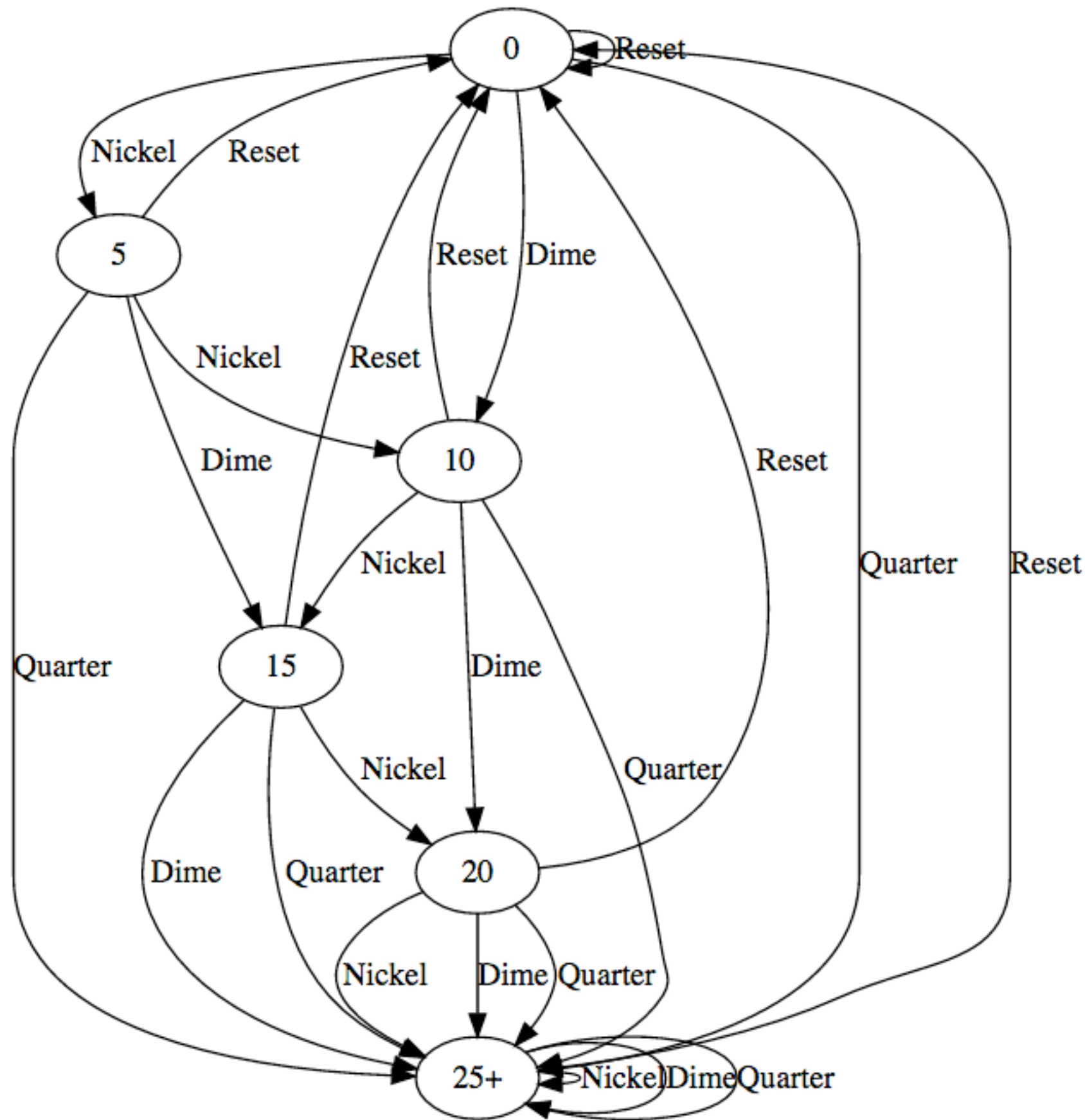


Significance

- Can encode many problems using finite state machines (FSMs)
- FSMs can be implemented with sequential circuits
- Internals of processors can be encoded with FSMs

Significance

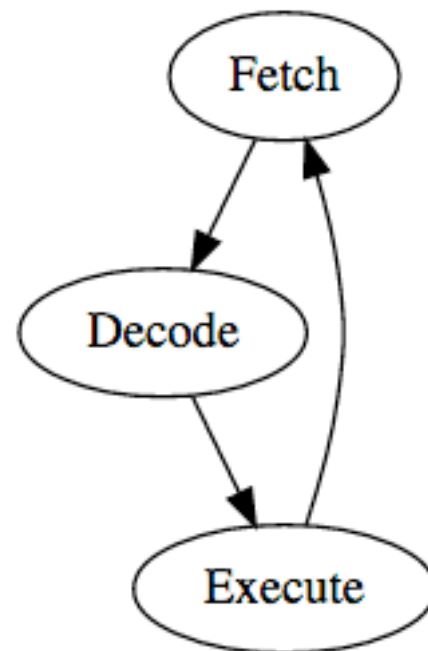- Can encode many problems using finite state machines (FSMs)
- FSMs can be implemented with sequential circuits
- Internals of processors can be encoded with FSMs




FSMs to Circuits

Step 1: Encode each state in binary


FSMs to Circuits

Step 1: Encode each state in binary

 

FSMs to Circuits

Step 1: Encode each state in binary

 


FSMs to Circuits

Step 2: Make truth table mapping current state to next state


FSMs to Circuits

 Step 2: Make truth table mapping current state to next state



FSMs to Circuits

 Step 2: Make truth table mapping current state to next state



S1	S0	N1	N0
0	0	0	1
0	1	1	0
1	0	0	0
1	1	X	X


FSMs to Circuits

Step 3: Simplify truth table (with Boolean algebra / K-maps)

FSMs to Circuits

Step 3: Simplify truth table (with Boolean algebra / K-maps)


S1	S0	N1	N0
0	0	0	1
0	1	1	0
1	0	0	0
1	1	X	X

 

FSMs to Circuits

Step 3: Simplify truth table (with Boolean algebra / K-maps)


S1	S0	N1	N0
0	0	0	1
0	1	1	0
1	0	0	0
1	1	X	X

 

FSMs to Circuits

Step 3: Simplify truth table (with Boolean algebra / K-maps)

S1	S0	N1	N0
0	0	0	1
0	1	1	0
1	0	0	0
1	1	X	X

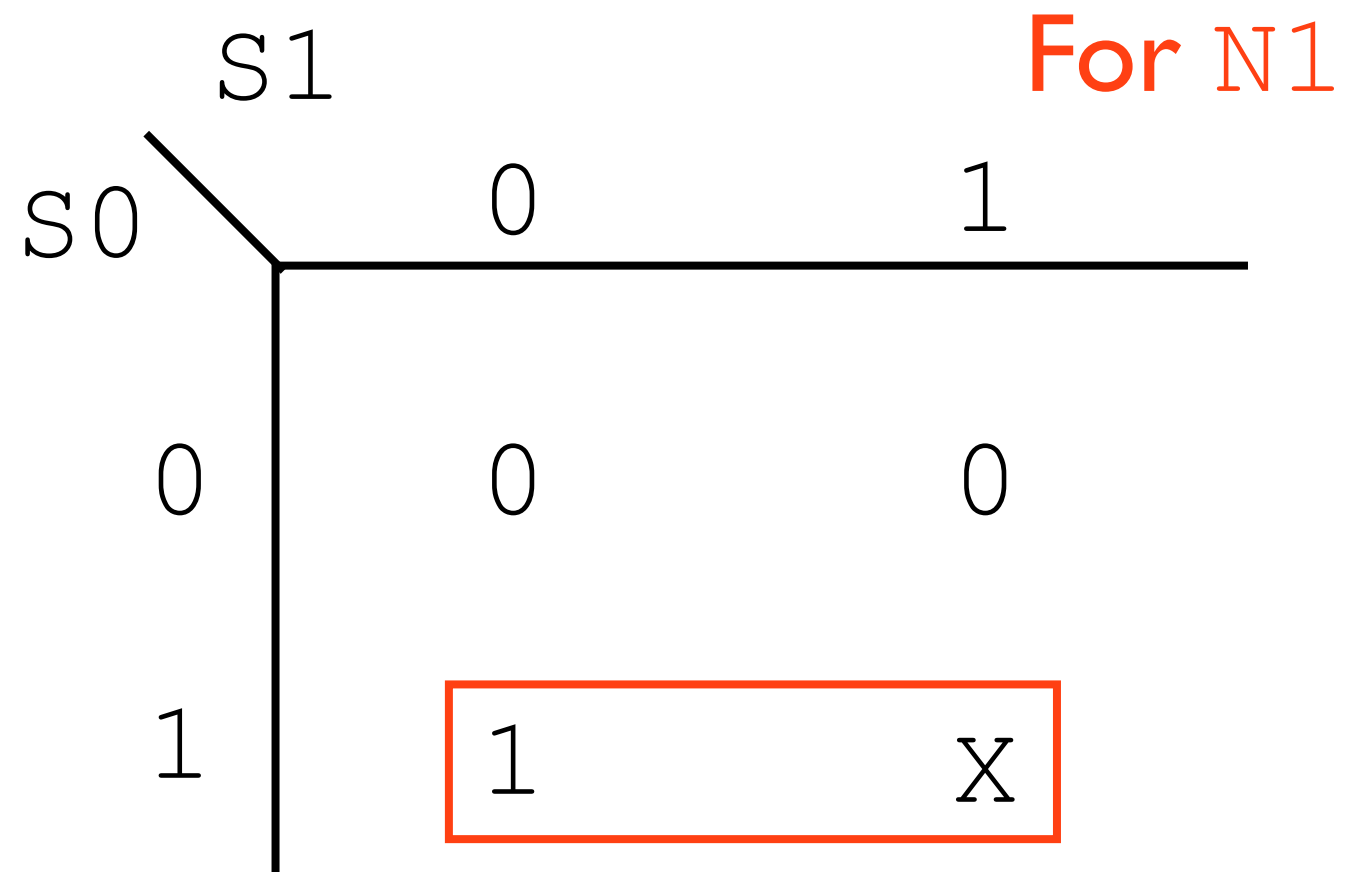

$$N1 = S0$$

FSMs to Circuits

Step 4: Build sequential circuit

FSMs to Circuits

Step 4: Build sequential circuit

S1	S0	N1	N0
0	0	0	1
0	1	1	0
1	0	0	0
1	1	X	X

$$N0 = \neg S1 \neg S0$$

$$N1 = S0$$


FSMs to Circuits

Step 4: Build sequential circuit

S1	S0	N1	N0
0	0	0	1
0	1	1	0
1	0	0	0
1	1	X	X

$$N0 = !S1 !S0$$

$$N1 = S0$$

 


FSMs with External Inputs

Same process, but with more inputs in the truth table


FSMs with External Inputs

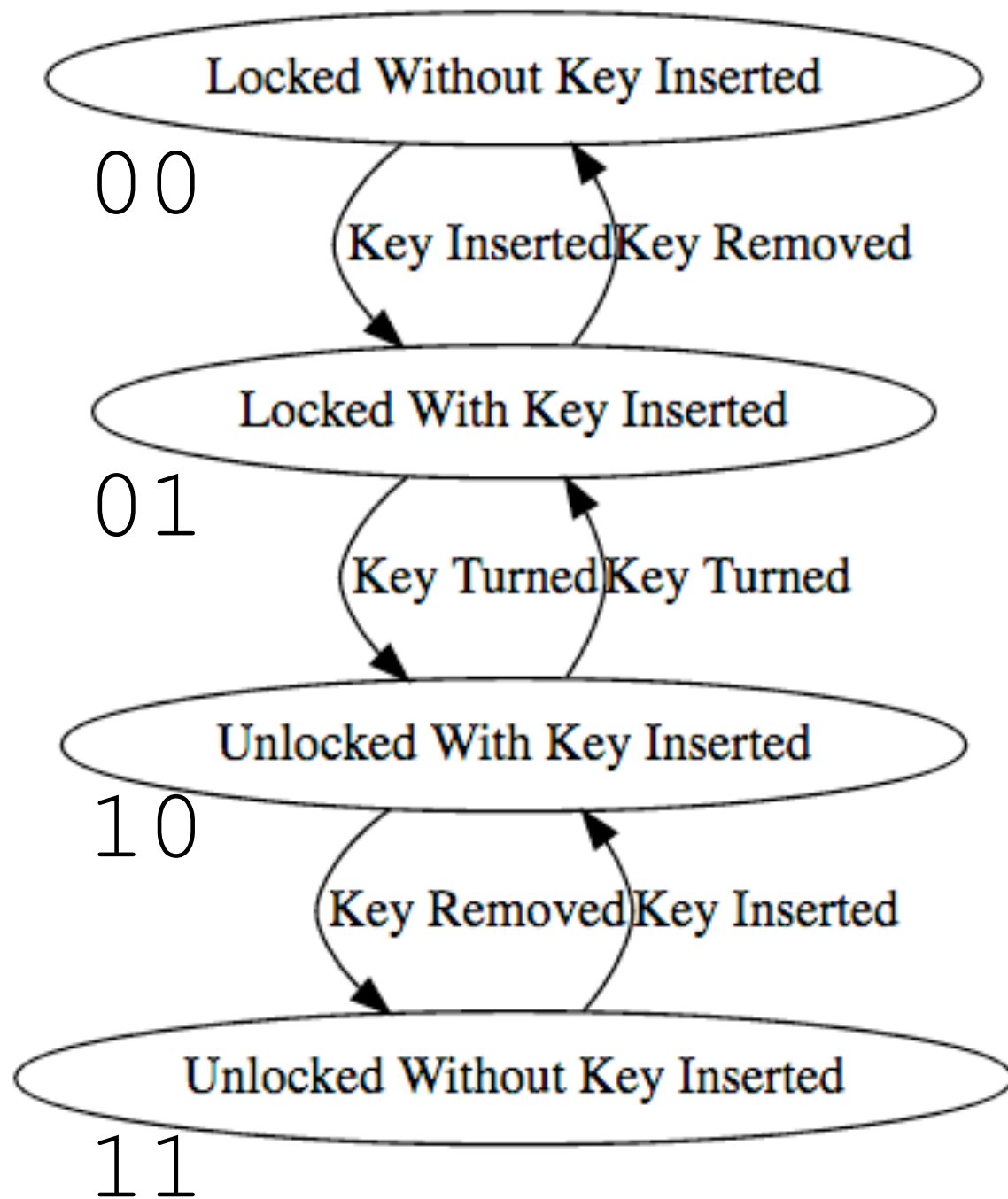Same process, but with more inputs in the truth table



FSMs with External Inputs

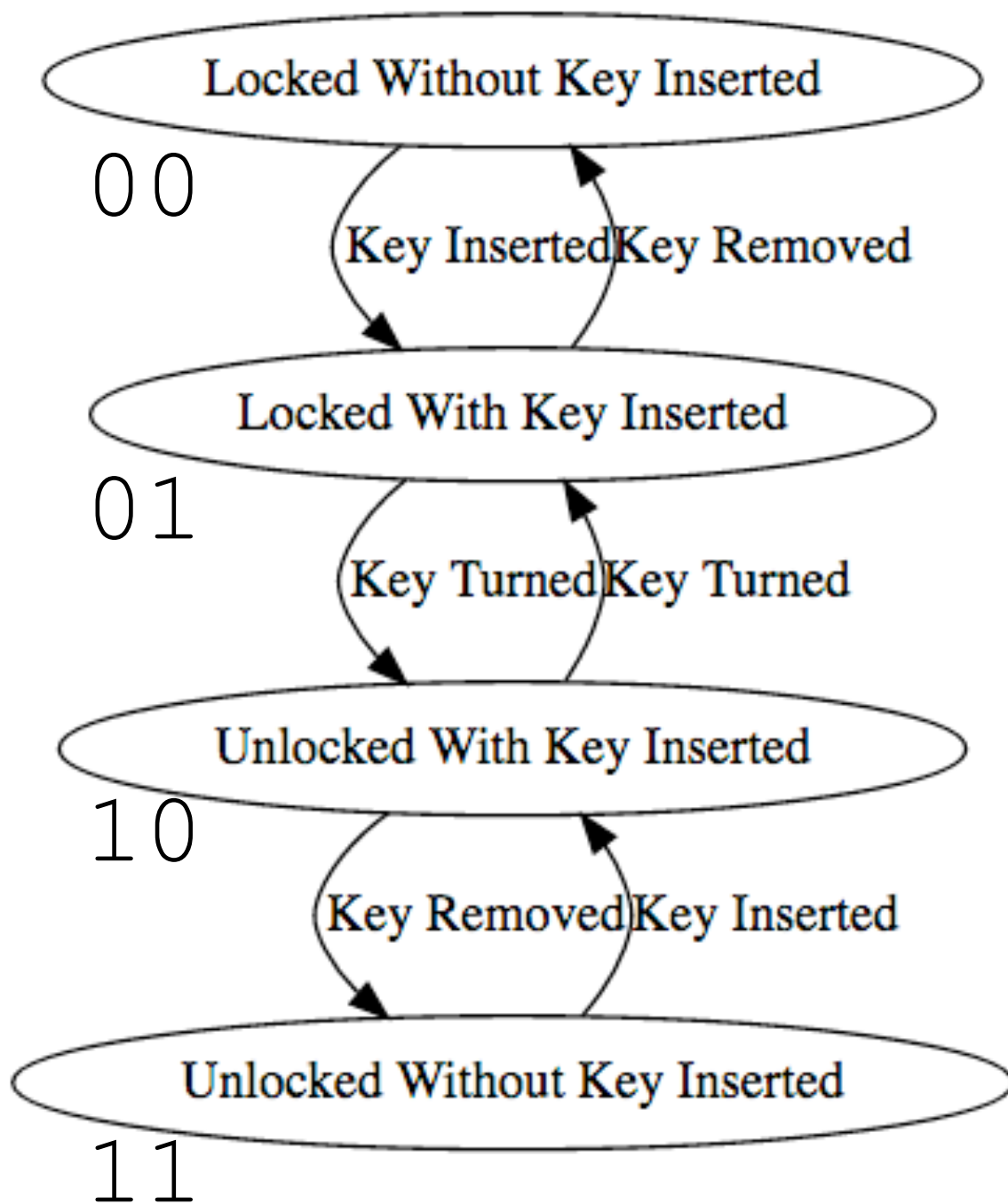Same process, but with more inputs in the truth table



KI	KR	KT	S1	S0	N1	N0
0	0	0	0	0	0	0
..
1	0	0	0	0	0	1
..


FSMs with Outputs

Additional outputs in truth table.

Output on the corresponding state.


FSMs with Outputs

 Additional outputs in truth table.
Output on the corresponding state.



FSMs with Outputs

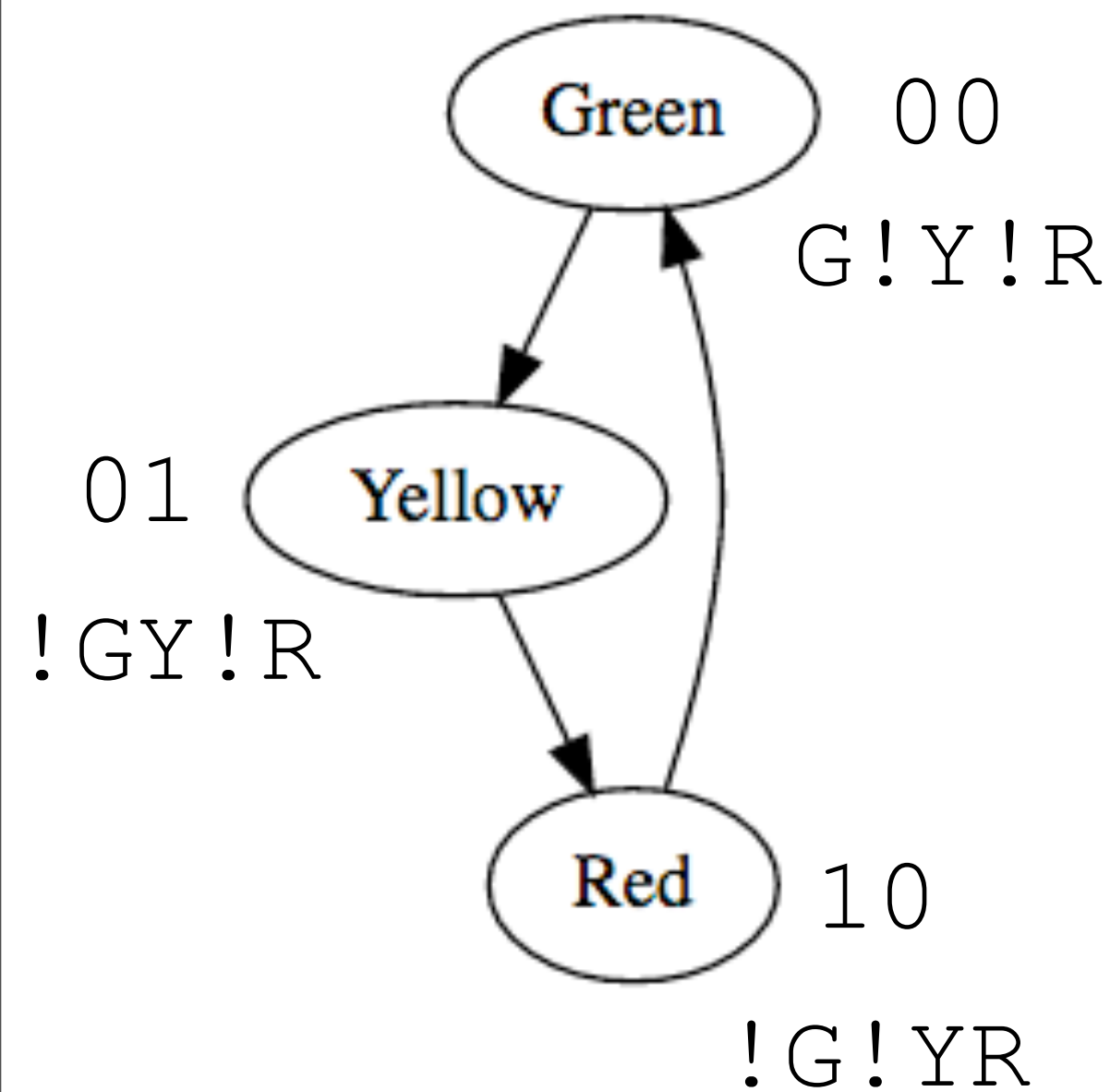
Additional outputs in truth table.
Output on the corresponding state.



FSMs with Outputs

Additional outputs in truth table.

Output on the corresponding state.

 

S1	S0	N1	N0	G	Y	R
0	0	0	1	1	0	0
0	1	1	0	0	1	0
1	0	0	0	0	0	1
1	1	X	X	X	X	X